



**THE FIRE ALARM  
NETWORK**

**EPISODE 01**

# FIRE ALARM FUNDAMENTALS

Quick Reference & Study Guide

- System components and their functions
- Normal, alarm, supervisory, and trouble
- Conventional Class B IDC supervision
- Practice questions with an answer key

**BEGINNER TRAINING | FREE LEARNING RESOURCE**

Companion to: Fire Alarm Systems Explained | Beginner Training (Episode 1)

Conceptual education only. Not a wiring, code-compliance, or installation manual.



---

THE SYSTEM AT A GLANCE

## Detect > Process > Notify & Respond

### INPUT

Devices detect a condition or a person initiates an alarm.

### CONTROL

The FACU evaluates signals and applies the sequence of operations.

### OUTPUT

Notification and other programmed building functions may operate.

## Know the major components

### Fire alarm control unit (FACU)

- Receives and interprets signals
- Displays system conditions
- Controls outputs per programmed operation
- Uses primary and secondary power

### Initiating devices

- Smoke: responds to smoke conditions
- Heat: responds to temperature
- Manual pull: allows human initiation
- Conventional zones vs. addressable points

### Notification appliances

- Horns: audible alert
- Strobes: visual alert
- Speakers: voice messages and tones
- Speaker circuits differ from typical horn/strobe NACs

### Other system interfaces

- Signals may go to a supervising station
- Door holders or elevator controls may operate
- Responses depend on design and programming
- Not every alarm activates every output

### Remember

An initiating device provides an input; a notification appliance provides an occupant alert.



---

**SYSTEM CONDITIONS**

## Four conditions you must distinguish

### **NORMAL**

No active alarm, supervisory, or trouble condition reported. Monitoring continues.

### **ALARM**

A fire alarm input is received and processed; required responses may operate.

### **SUPERVISORY**

A monitored fire protection system or related equipment needs attention; e.g., a valve off normal.

### **TROUBLE**

A fault or abnormal condition is reported; e.g., open circuit, ground fault, AC loss, or battery issue.

## Important distinctions

- Supervisory is not automatically a fire alarm.
- Trouble does not by itself establish that a fire exists.
- More than one condition can be displayed simultaneously.
- Colors in this guide: normal = green; alarm = red; supervisory/trouble = amber.




## CONVENTIONAL IDC SUPERVISION

# How a simplified Class B IDC works

Illustrative circuit: two conductors, a normally-open pull-station contact, and an EOL resistor.

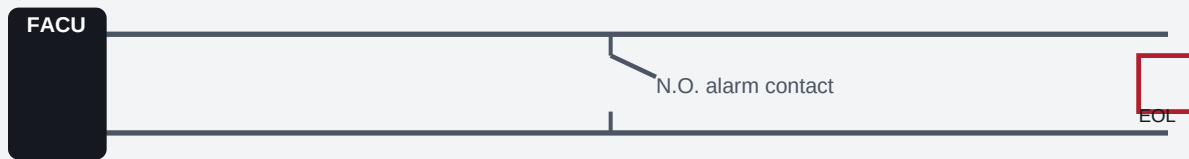
### NORMAL

Contact open; panel sees the EOL resistance.



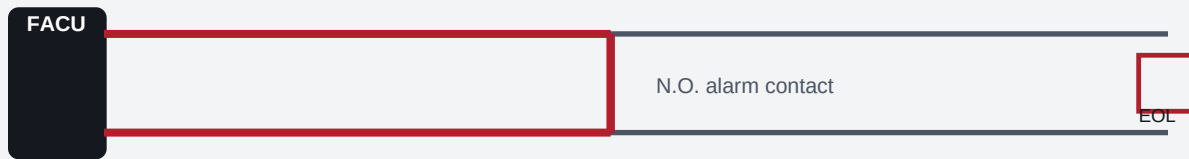
### ALARM

Contact closes, creating a lower-resistance parallel path.


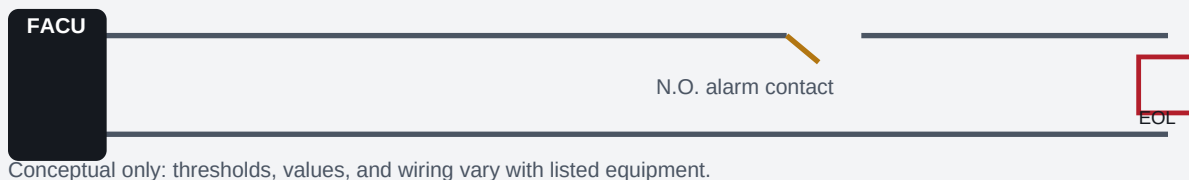
### OPEN TROUBLE

With no alarm contact closed, a conductor break prevents EOL supervision.



## Technical note

Closing the contact does not physically remove the EOL; the dominant current path shifts.



**KNOWLEDGE CHECK**

## Check your understanding

1. Which component receives input signals and determines system responses?

---

2. A sprinkler control valve moves away from its normal position. Which signal may result?

---

3. An open occurs before the EOL in the simplified Class B IDC, contact open. What results?

---

4. Name one difference between an initiating device and a notification appliance.

---

5. What electrical element allows a typical resistor-supervised IDC to distinguish normal from open?

---



**ANSWER KEY AND NEXT STEPS**

# Answers & explanations

## QUESTION 1

Fire alarm control unit (FACU).

## QUESTION 2

Supervisory signal.

## QUESTION 3

Trouble condition.

## QUESTION 4

Initiating device provides a monitored input; notification appliance alerts occupants.

## NEXT LESSON

### Basic Electrical Principles for Fire Alarm Technicians

Voltage, current, resistance, and how they relate to fire alarm circuits.

[thefirealarmnetwork.com](http://thefirealarmnetwork.com) | [youtube.com/@TheFireAlarmNetwork](https://youtube.com/@TheFireAlarmNetwork)